
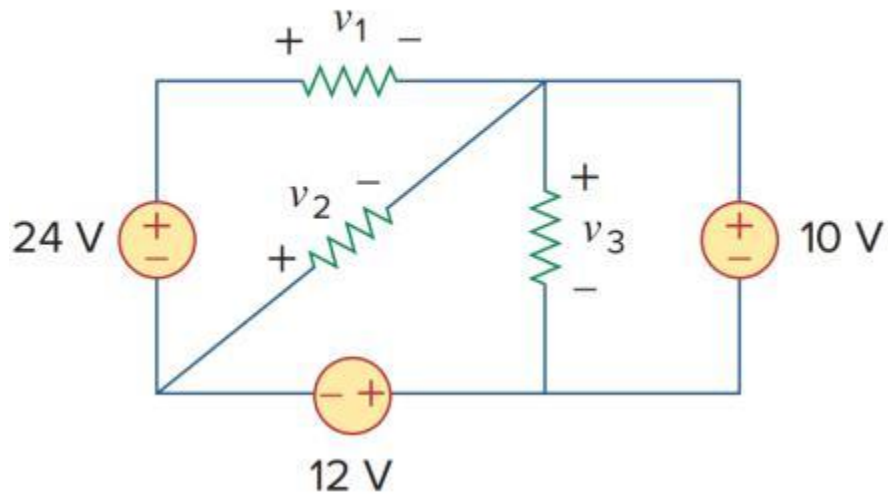


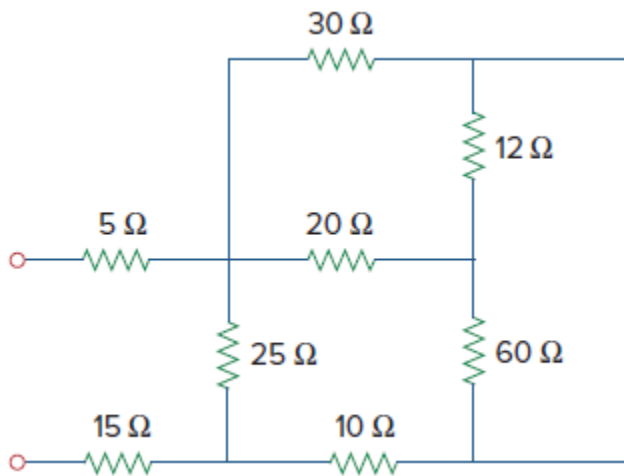1.

Obtain v_1 through v_3 in the following circuit.




2. Find the equivalent resistance at terminals $a-b$




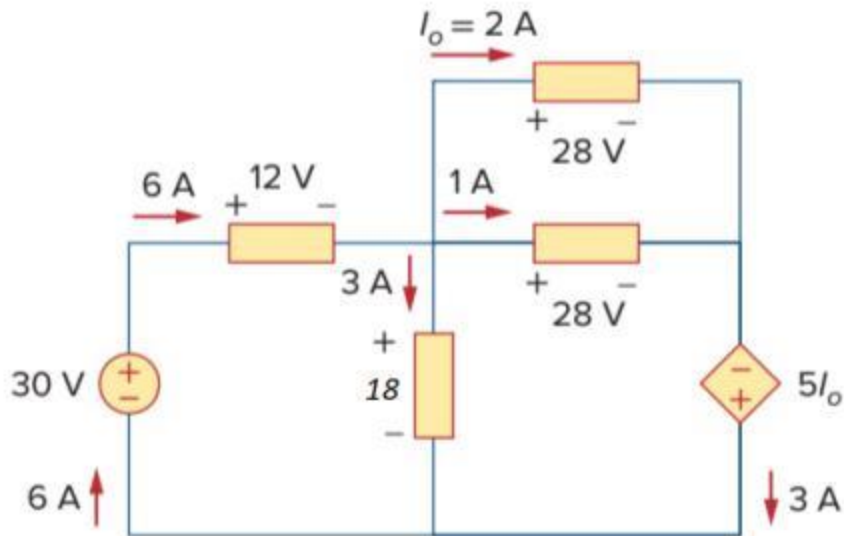3.

Find the power supplied/absorbed by each of the elements shown in the circuit below.



4. Find v_o and i_o in the circuit

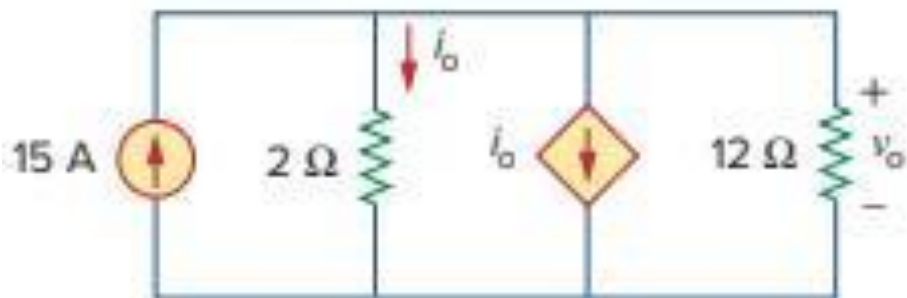

5. Find R_{ab} for the circuit shown below.

