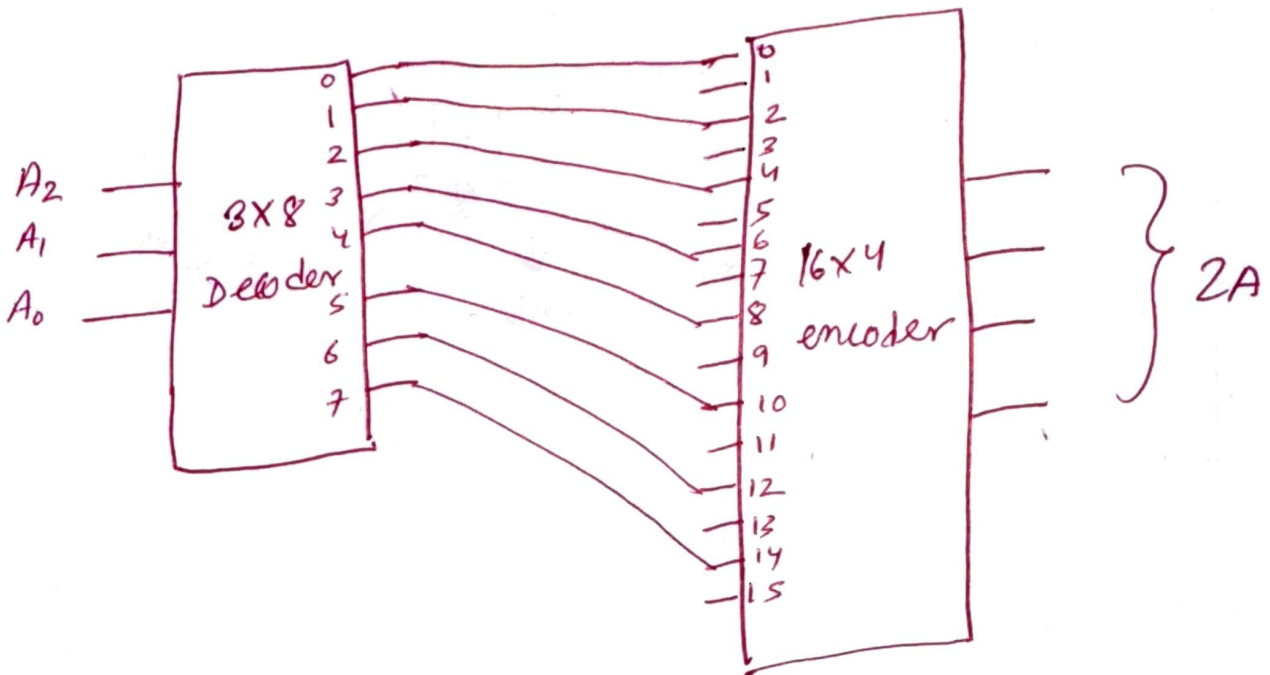


Name: <i>Solution</i>	ID:	Section:
-----------------------	-----	----------

1.CO3	Consider A is a 3-bit binary number. Design a circuit which converts A to 2A using appropriate sized decoders and encoders. The output 2A will be a 4-bit number.	6
2.CO3	Build the following function using exactly five 8:1 Mux(s). $F(A,B,C,D,E) = \Sigma (3,5,9,11,16,21,24,28)$	9



will be a 4-bit number.

2)

