



CSE260: Digital Logic Design
Summer 2025
Quiz - 03
Duration: 25 minutes

B

Name:	ID:	Section:
-------	-----	----------

1.CO3	Consider A is a 3-bit binary number. Design a circuit which converts A to 2A using appropriate sized decoders and encoders. The output 2A will be a 4-bit number.	6
2.CO3	Build the following function using both 16:1 Mux(s) and 4:1 Mux(s). Your solution should be efficient, meaning it must use the least number of components. $F(A,B,C,D,E) = \Sigma (1,2,4,7,12,13,18,19,26,30)$	9

same as set-A

