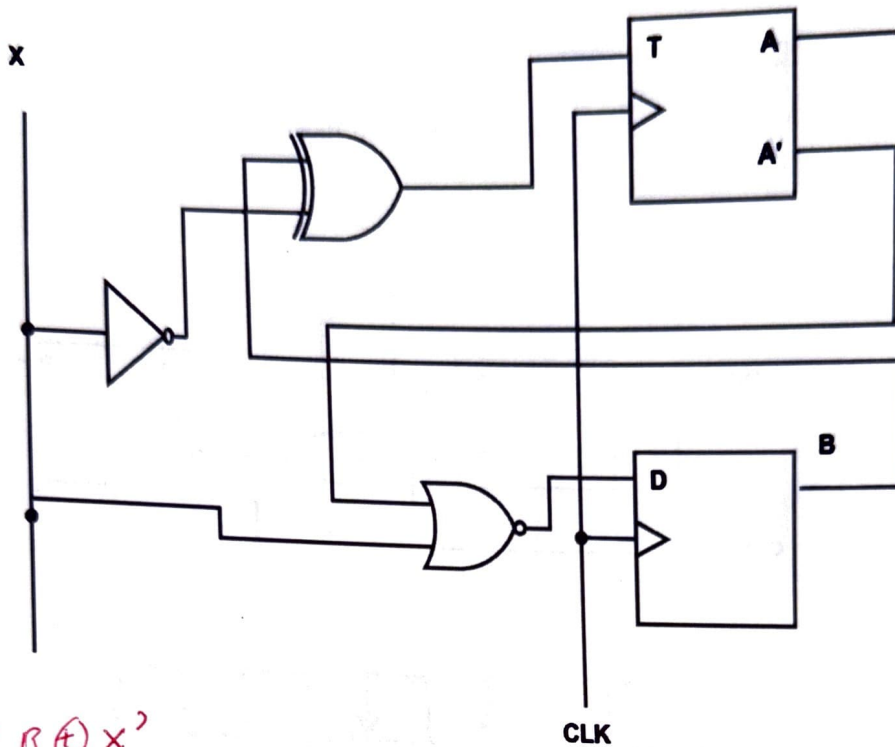


$$JB = A$$

2. Convert the Circuit diagram to a state diagram.



$$TA = B \oplus X'$$

$$DB = (A' + X)' = A \cdot X'$$

A	B	X	TA	DB	A+	B+
0	0	0	1	0	1	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	1	0	1	0
1	0	0	1	1	0	1
1	0	1	0	0	1	0
1	1	0	0	1	1	1
1	1	1	1	0	0	0

