



CSE260 Summer 2025

Assignment 4


Total: 20

This assignment must be handwritten. Show ALL steps in ALL questions.

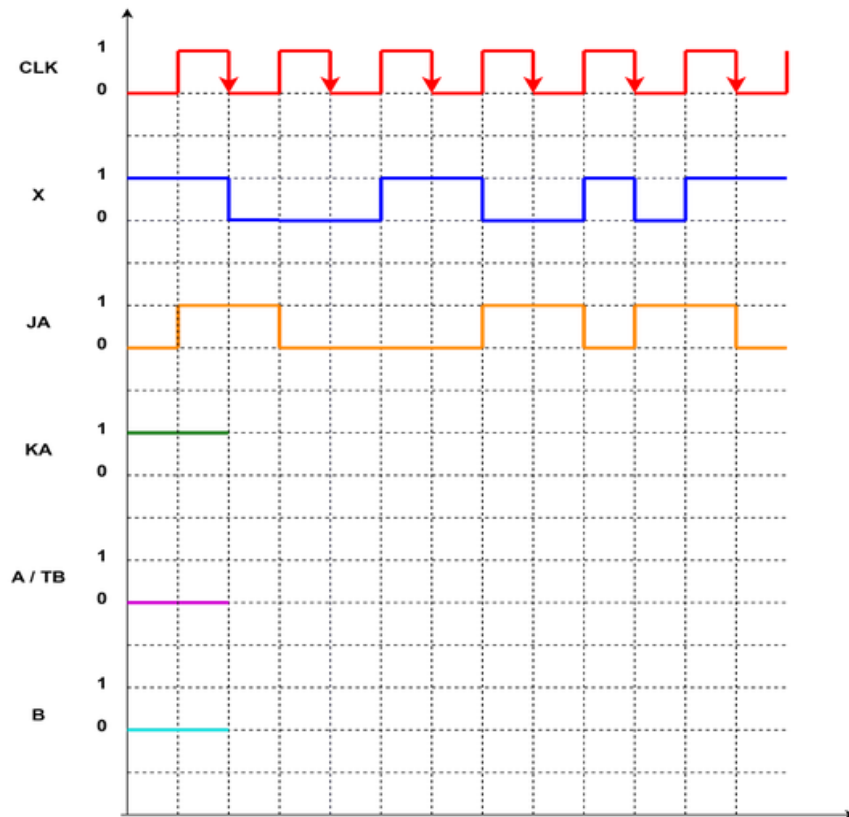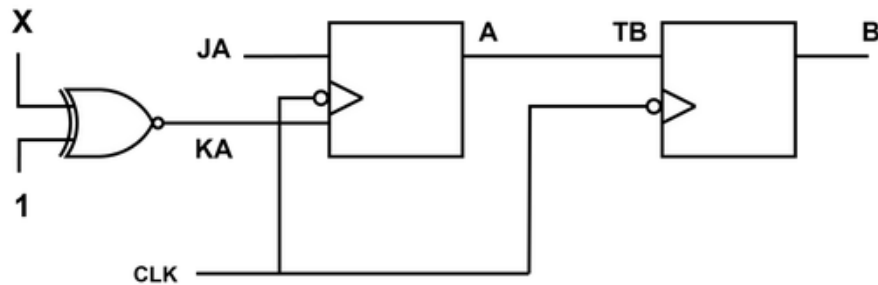1. [5 Marks] Draw and complete the **timing diagram** for the following circuit, where all the flip-flops are **negative-edge-triggered**. Clock Pulse(CLK), JA, and X waveforms are given.



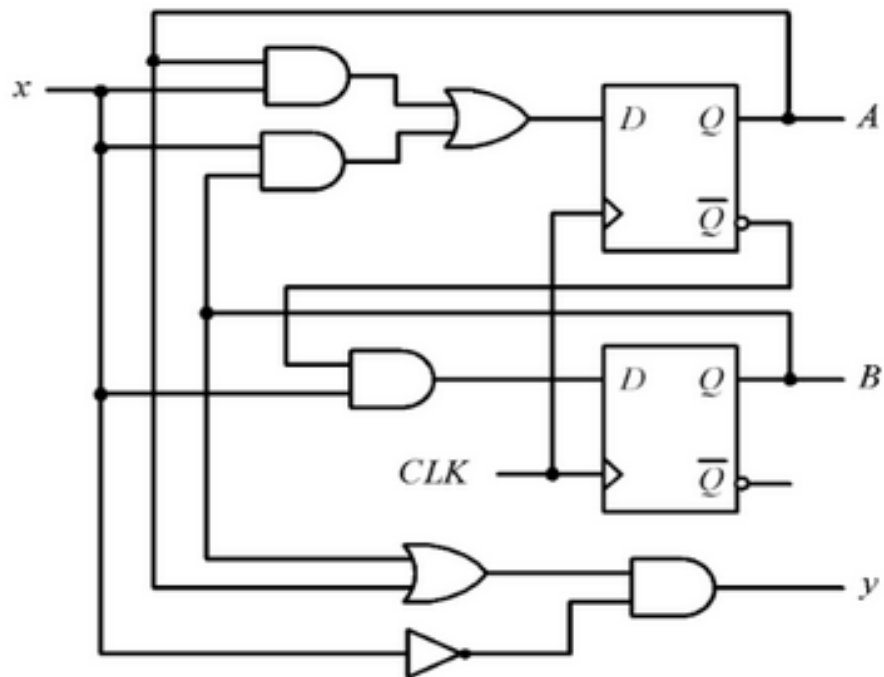2. [7 Marks] Draw the state diagram for the given circuit. Show all intermediate steps.



3. [8 Marks] Implement the following counter using **JK FF**. Show all steps.

Green->Orange->Yellow->Red->Yellow->Orange->Yellow->Green