

BRAC University (Department of Computer Science and Engineering)
CSE260 Summer 2025

Examination: Quiz 4

Duration: 20 Minutes

Full Marks: 18

Name: _____

ID: _____


Section: _____

Answer the following questions. You **MUST** show your workings/calculations where applicable.

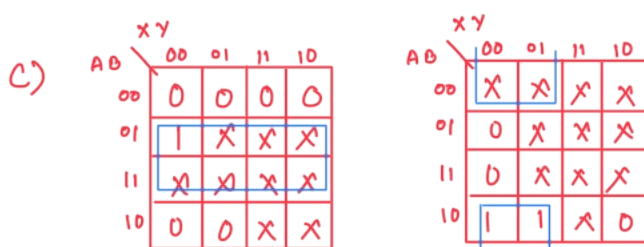1. Implement the following sequence counter using **SR** flip flop(s):

CSE110 → CSE111 → CSE220 → CSE221 → CSE220 → CSE111 → CSE220 → CSE110

- Show the state diagram. [3]
- Show the state table. [5]
- Derive the equations using K-Maps. [5]
- Show the final circuit diagram. [5]



You can follow both way (Don't care or fixed transition) But follow one method!

