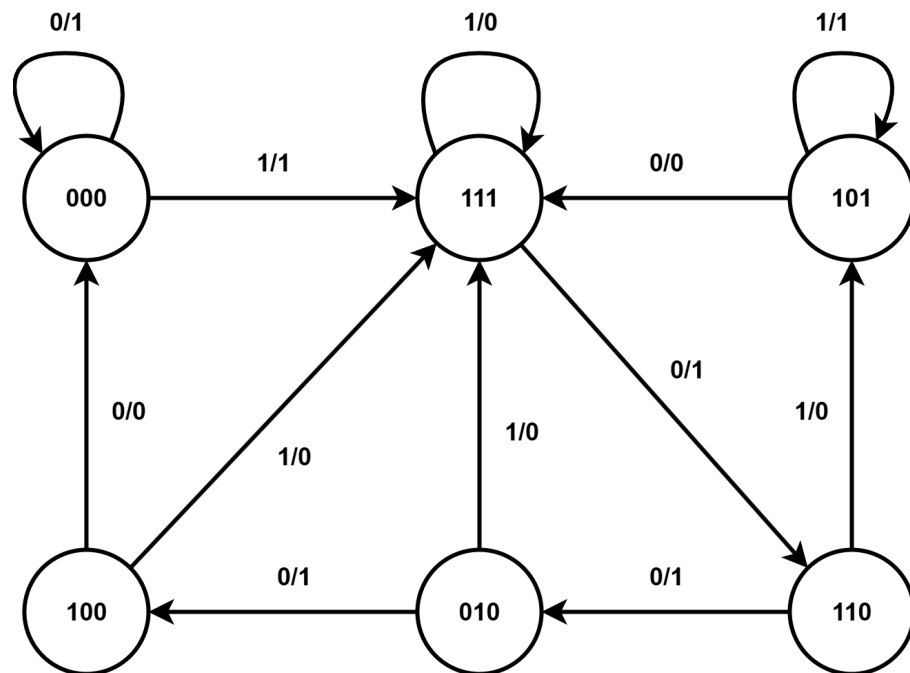


Assignment 4

1. Construct the circuit diagram using JK Flip-flops for the following state diagram. [For any invalid states, use don't cares as output of any operation for that invalid state] [Marks: 10]



2. Now, only replace the JK Flip-flops with SR Flip-flops in your circuit diagram. Build the state diagram for the modified circuit diagram. [Marks: 10]