


CSE260

Assignment 04

This assignment must be hand-written. Show ALL steps in ALL questions

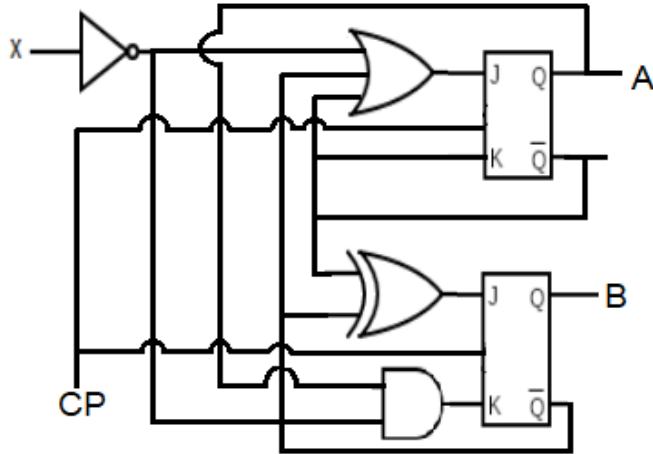
Question 1

Draw the state diagram for the following circuit:



[Ungraded - Recommended for practice]

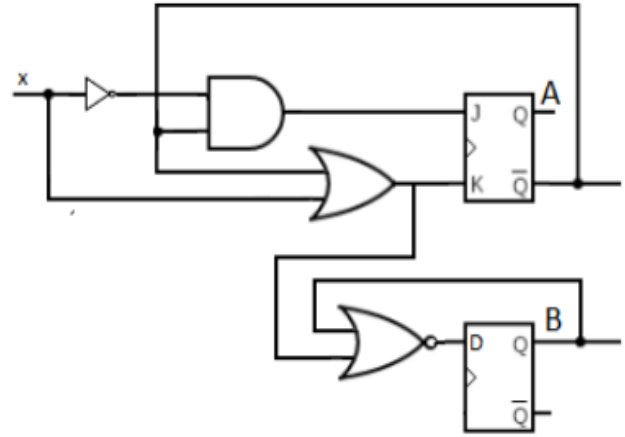Draw the state diagram for the following circuit:



[Ungraded - Recommended for practice]

Draw the state diagram for the following circuit:

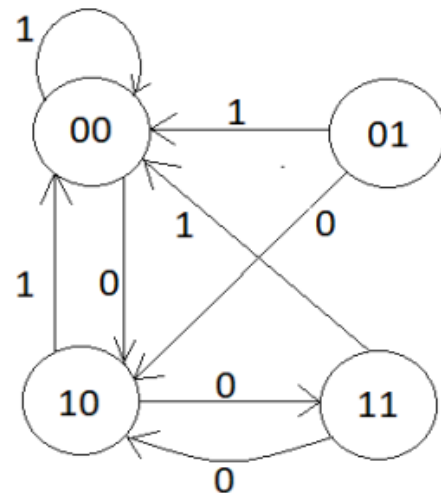
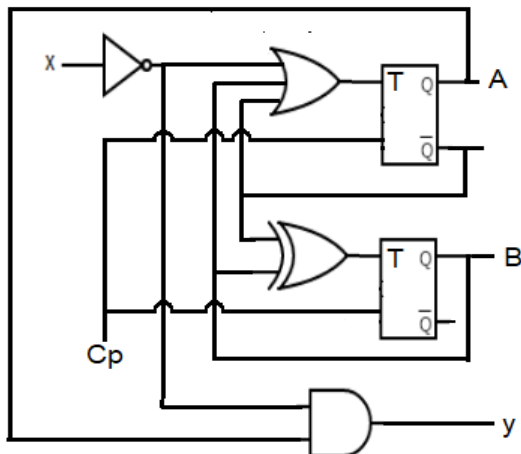


Figure: 1

Question 2:

Given the state diagram [Figure 1], get the sequential circuit using:

- SR Flip-Flop
- T Flip-Flop [Ungraded - Recommended for Practice]

Question 3:

3->5->7->11->12->14->3 Implement the given counter using:

- JK flip-flop.
- D flip-flop. [Ungraded - Recommended for Practice]

Question 4:

Implement 2 bits up/down counter using T flip flop

Question 5:

Implement the following counter using D flip flop

PHY111 - PHY112 - CSE250 - CSE251 - CSE260 - CSE340 - CSE341 - PHY111