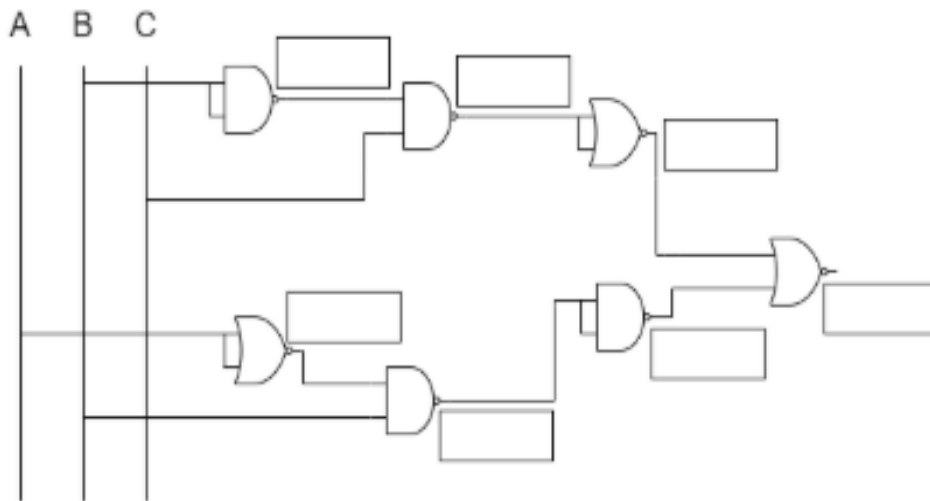


CSE260 Assignment 02
[C02]
Total Mark: 25
Deadline: July 21, 2025; 11:59PM
Submission Link: [Click Here](#)

This assignment must be hand-written. Show ALL steps in ALL questions.

1. Convert the following function to its corresponding canonical **SOP** form using boolean laws. Also, write down the **Minterms** of the function. $F(w,x,y,z) = (xy + z)(y + xy' + yz)$
2. Convert the following function to its corresponding canonical **POS** form using the distributive laws. Also, write down the **Maxterms** of the function. $F(x, y, z) = (xy + z)(xy' + yz)$
3. Determine the logic function of the below circuit. Use the boxes in the diagram to write your answer step by step.



4. Given that the max terms of the function $F(A, B, C)$ are $M(0,2,4)$, complete the remaining POS expression by filling in the gaps:
 $F = (A+B+C)(A+ _ + C)(?)$
5. Draw an XOR gate using NOR gates only