

Name:	ID:	Section:
-------	-----	----------

Design the state diagram for the following circuit diagram. Show all necessary and relevant tables and equations. [15 Mark]

