

CSE260


Assignment 04

This assignment must be hand-written. Show ALL steps in ALL questions

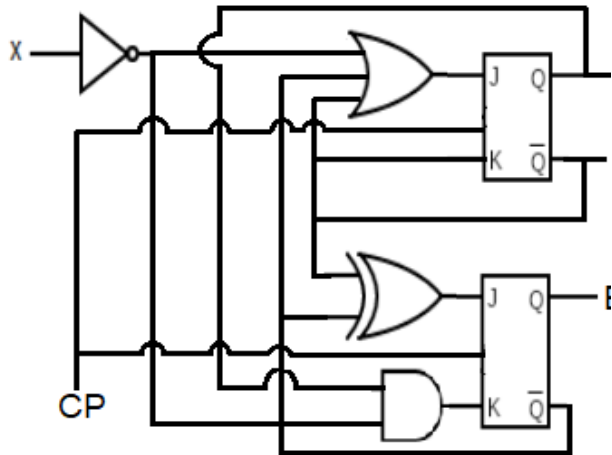
Question 1

[Ungraded - Recommended for practice]

Draw the state diagram for the following circuit:



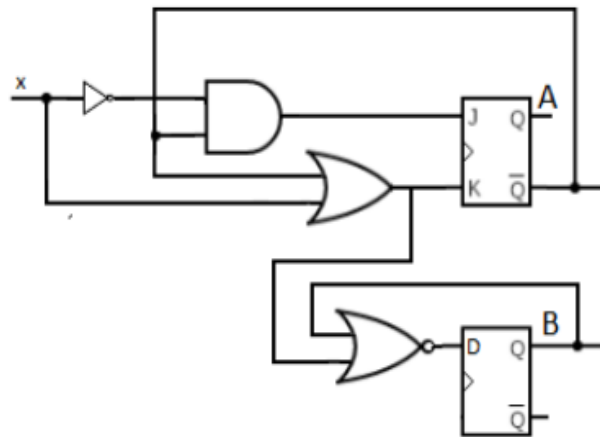Draw the state diagram for the following circuit:



[Ungraded - Recommended for practice]

Draw the state diagram for the following circuit:

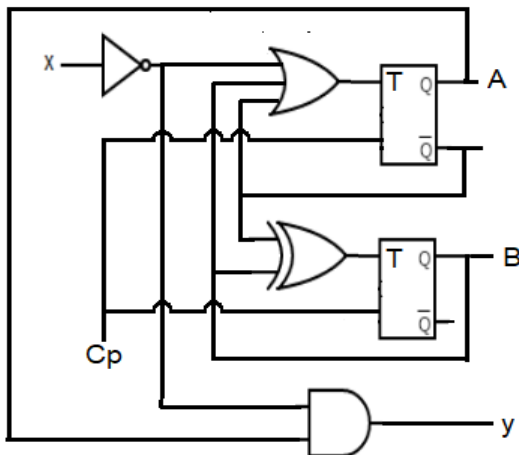


Figure: 1

Question 2:

3->5->7->11->12->14->3 Implement the given counter using:

- JK flip-flop.
- D flip-flop. **[Ungraded - Recommended for Practice]**

Question 3 :

Implement the following counter using T FF:

Leon->Claire->Leon->Ada->Chris->Leon->Chris->Ada->Claire

Note: You have to show all the necessary tables including all the tables of the mentioned flip-flops, you also have to make the circuit efficient

Question 4:

Complete the timing diagram using the following circuit:

