



Assignment 04

Deadline: 7

September, 2025

This assignment must be hand-written. Show ALL steps in ALL questions.

You only need to submit question 4. All the other questions are ungraded and are recommended for practice.

5. Implement the following counter using T flip flop

**CSE110-> CSE111-> CSE220-> CSE221->
CSE331-> CSE221-> CSE321-> CSE110**

6. 3->4->6->10->12->13->15->3

i. Implement the given counter using **JK flip-flop**.

ii. Implement the given counter using

T flip-flop

NB: For states not given in the question, please move to the initial state as per the question.

7. Implement 4 bit up/down counter using JK flip-flop

**8. Implement the following counter using JK FF:
Green->Yellow->Red->Yellow->Green**

**9. Implement the following counter using T FF:
Green->Orange->Yellow->Red->Yellow
->Orange->Yellow->Green**

**10. Implement the following counter using JK FF:
1->2->3->5->7->11->13->1**